



MANIPAL
UNIVERSITY
JAIPUR

SCHOOL OF COMPUTING & IT
Department of IT/ CSE/ CCE
III Semester; First Sessional Examination, Sept. 2016
Course: B.Tech
OPEN BOOK EXAMINATION

Subject Code: CS1302
Max. Marks: 20

Subject Name : Switching Theory & Logic Design
Duration : 1 hour

Instructions:

1. All questions are compulsory
2. Missing data if any can be suitably assumed
3. Numbers in [] indicates marks
4. Calculator is not allowed

Q1. Perform the following operations

- a) $(4310)_5$ to $()_{10}$
- b) $(435)_8$ to $()_{10}$
- c) $65 - 12$: BCD Subtraction using 9's complement.

[1]
[1]
[2]

Q2. (a) Show that the dual of the exclusive-OR is equal to its complement.

[2]
[2]

b) Simplify the following expression using Boolean postulates

$$(A + C)(AD + AD') + AC + C$$

Q3. Implement the following Boolean function F, together with the don't care conditions d, using NAND Gates only.

$$F(A, B, C, D) = \sum (2, 4, 10, 12, 14)$$

$$d(A, B, C, D) = \sum (0, 1, 5, 8)$$

[4]

Q4. Using the Quine McClusky method, Obtain the minimum sum of product expression of the following function with the don't care conditions d.

$$F(A, B, C) = \sum (0, 1, 4, 5, 6)$$

$$d(A, B, C) = \sum (2, 3, 7)$$

[4]

Q5. Design and Implement the Half Adder circuit using NOR Gates only.

[4]